

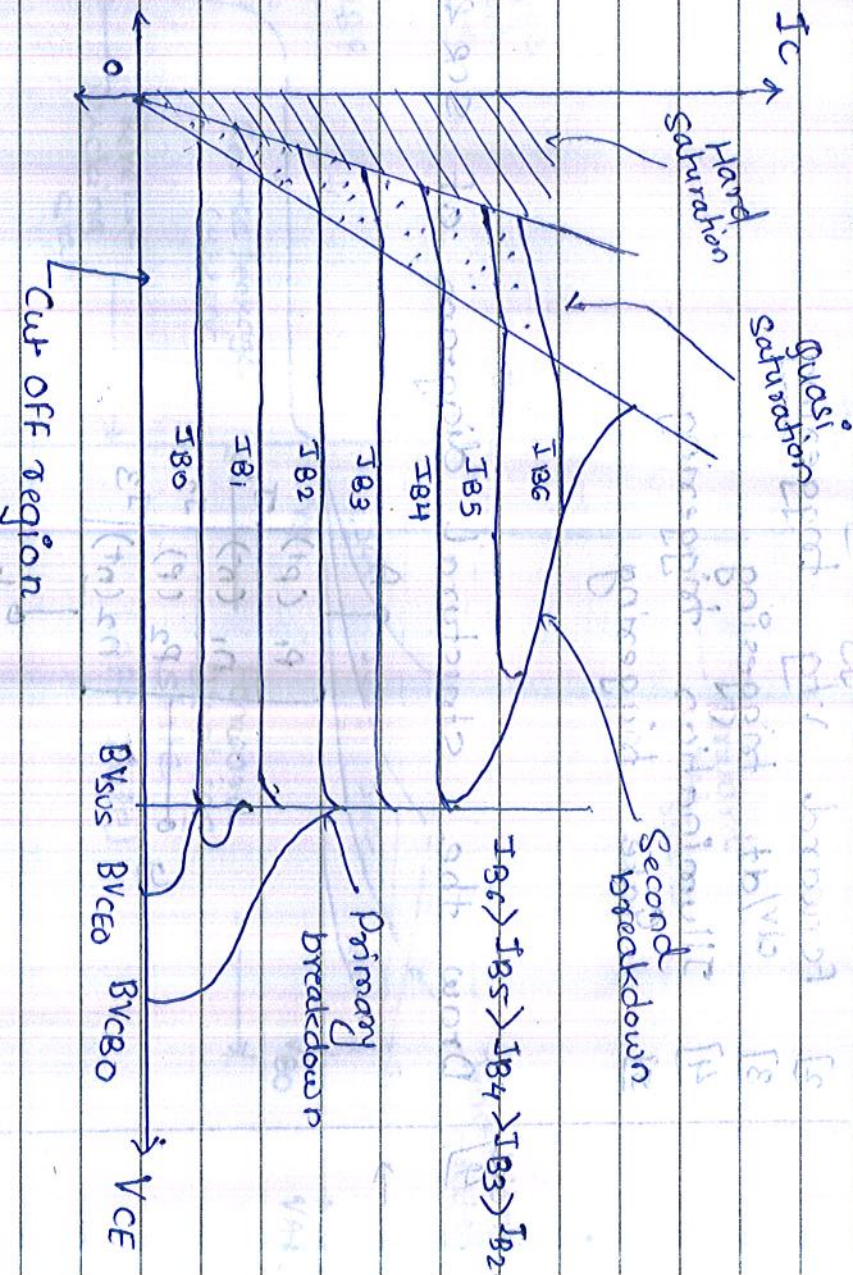
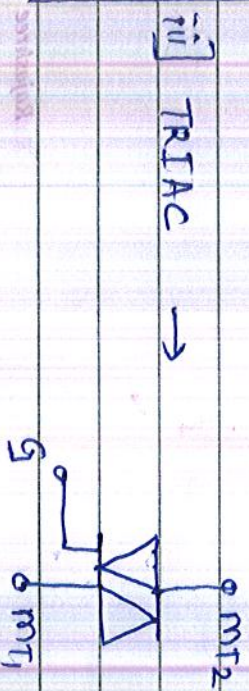


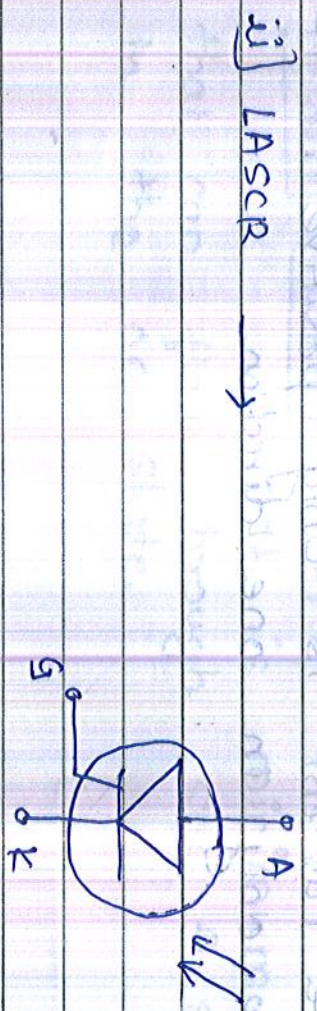Q.1] 1] Draw the labeled V-I characteristics of power transistor.



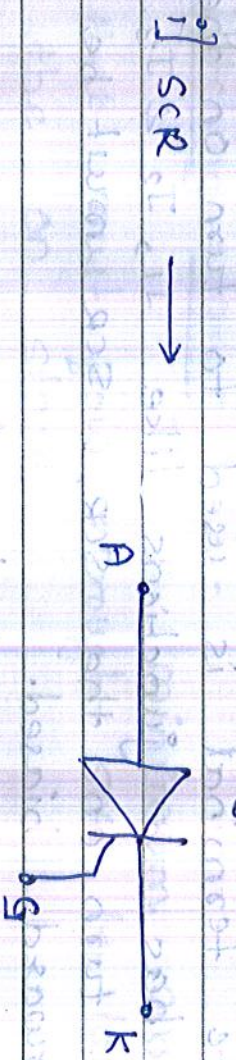
2] Draw the symbols of following devices.





3] List the different turn off on methods of SCR.

- 1] Thermal triggering
- 2] Forward Vtg triggering
- 3]  $dv/dt$  triggering
- 4] Illumination triggering.
- 5] Gate triggering.

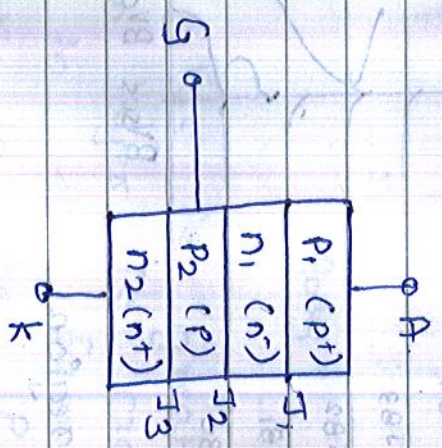4] Draw the structural diagram of SCR & explain.




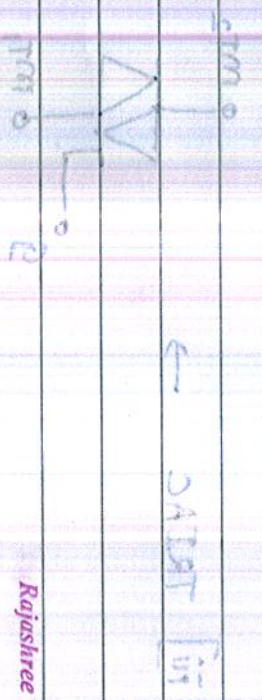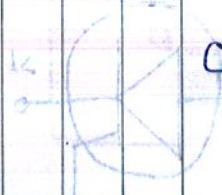- It is a 4 layer PNP structure.
- It has 3 terminals, anode, cathode & gate.
- Gate terminal is used to turn on the SCR.
- It has 3 junctions like J<sub>1</sub>, J<sub>2</sub> & J<sub>3</sub>.
- To turn on the SCR, SCR must be in forward biased.
- SCR is a unidirectional device.
- Gate current is only positive i.e. it can flow only in one direction.



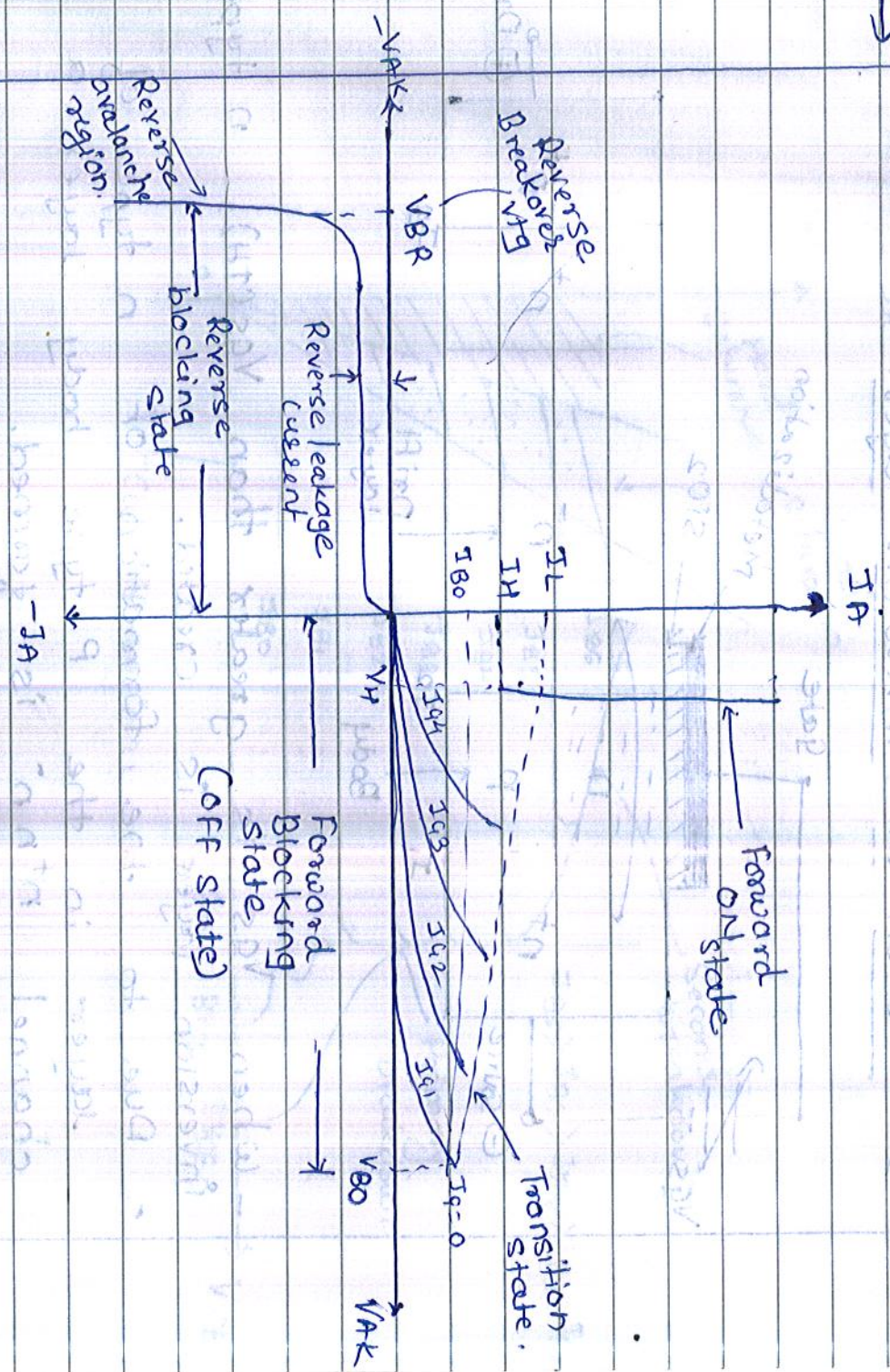Q.2]

i] Draw the V-I characteristics of SCR. Define latching current & holding current.



Latching current ( $I_L$ ):-


It is minimum anode current that must flow through SCR to latch it into the on state.

Holding current ( $I_H$ ):-

It is minimum current that can flow through SCR & still hold it in the on state.


2] Explain the operating principle of IGBT.

→ i] Creation of inversion layer.

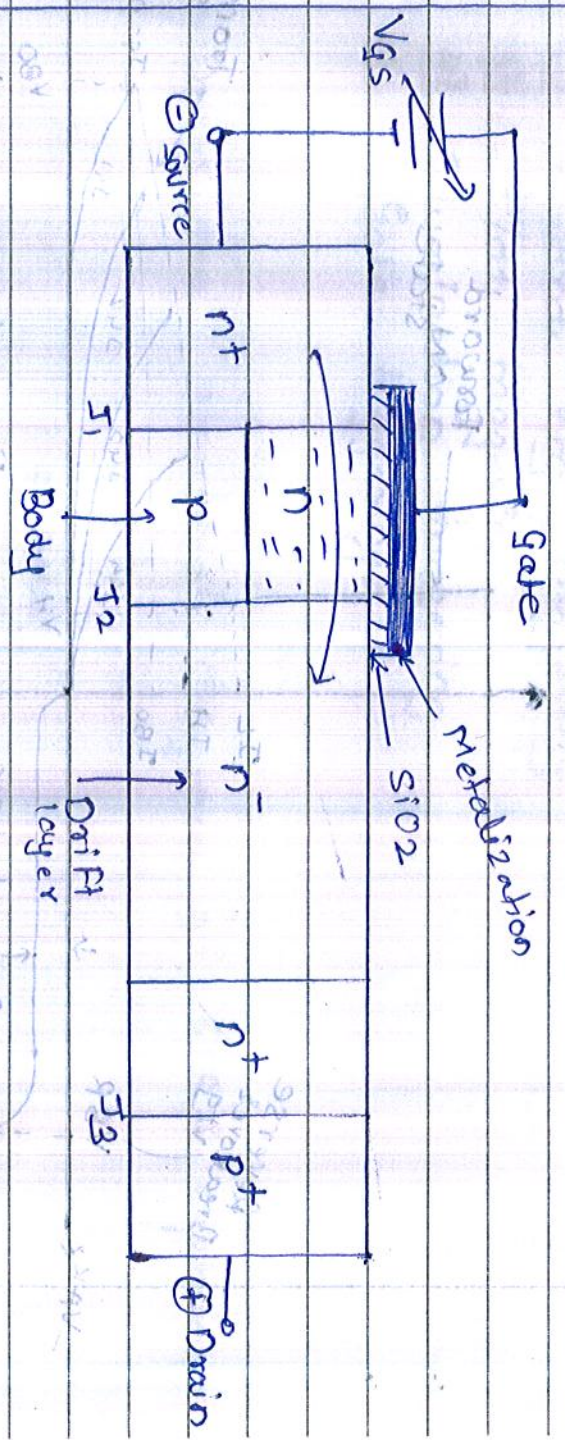


- when  $V_{gs}$  is greater than  $V_{gs(TH)}$ , n type inversion layer is created.
- Due to the formation of n type of layer in the p type body a channel  $n^+n^-$  is formed.


ii] Conductivity Modulation :-

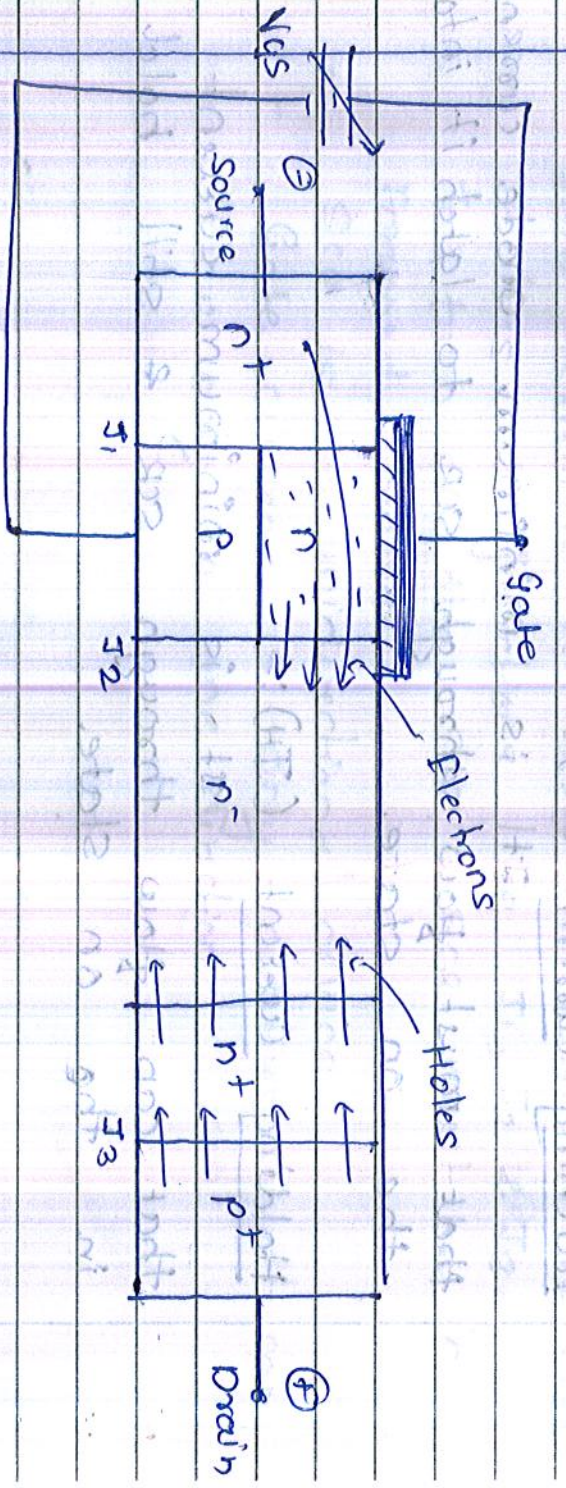

- when the forward v<sub>g</sub> bel<sup>n</sup> drain & source is applied, junction J<sub>3</sub> is forward biased.
- Due to creation of inversion layer electrons from the source are injected into the n<sup>-</sup> drift layer via n<sup>+</sup>p<sup>-</sup>n<sup>-</sup> junction.
- As the I<sub>a</sub> is forward biased it will inject holes in the n<sup>+</sup> buffer layer. The electrons injected in the n<sup>-</sup> drift layer create a space charge which will attract holes from the n<sup>+</sup> buffer layer which were injected by p<sup>+</sup> layer.
- So the double injection takes place into the n<sup>-</sup> drift region from both sides.
- This increases the conductivity of the drift region & reduces the resistance to its minimum.

3] Explain dv/dt triggering of SCR.

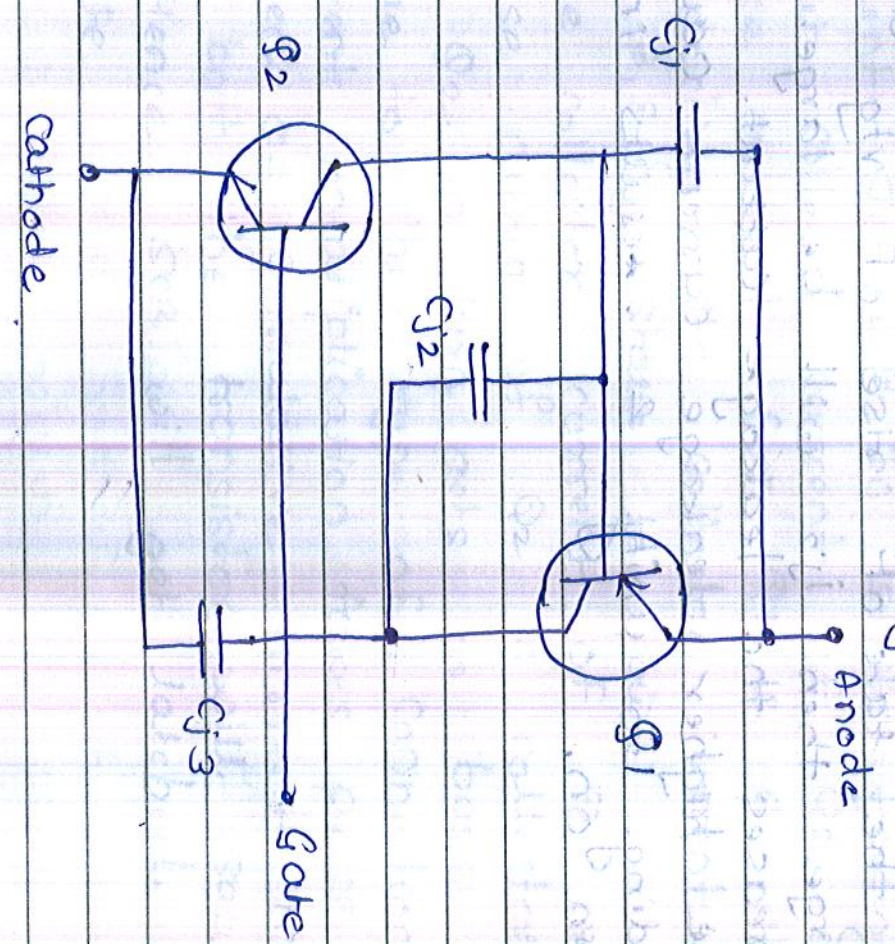

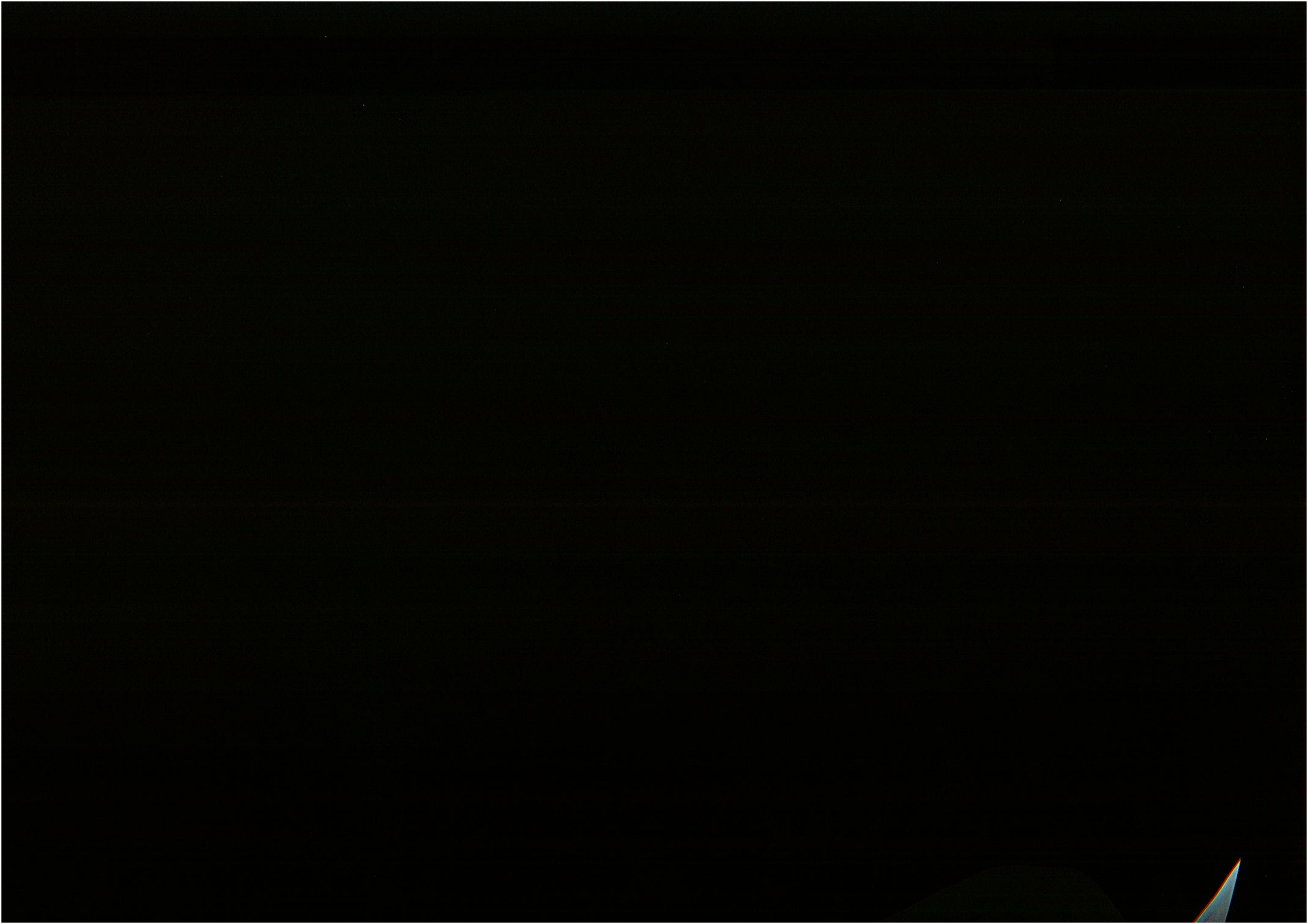

- Assume that  $I_g = 0$ , & suddenly apply a very high forward  $V_f$  bet<sup>n</sup> anode & cathode of a thyristor.
- Then it is said that rate of change of voltage i.e.  $dV/dt$ .
- Such a situation is called as transient operating condition.

The current through  $C_{j2}$  is

$$I_{j2} = \frac{d(Q_{j2})}{dt} = \frac{d(C_{j2}V_{j2})}{dt}$$


$$= V_{j2} \frac{dC_{j2}}{dt} + C_{j2} \frac{dV_{j2}}{dt}$$

where

- $C_{j2}$  - Capacitance of  $J_2$
- $V_{j2}$  - Voltage of  $J_2$
- $Q_{j2}$  - charge in the junction.

- If the rate of rise of  $V_f$   $\frac{dV}{dt}$  is large then  $j_2$  will be large. & this increases the leakage current.

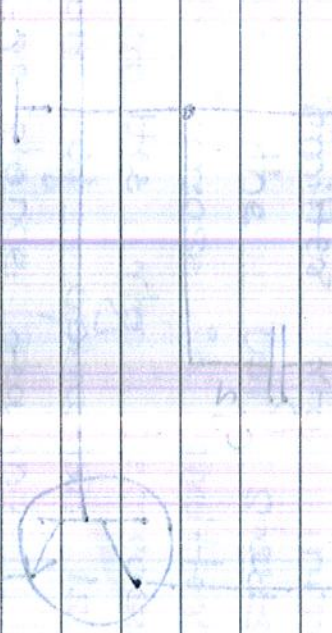- The higher leakage current causes  $(\alpha_1 + \alpha_2)$  tending to unity & results in SCR turn on.



- Assume that  $I_g = 0$ , & suddenly apply a very high forward  $V_f$  bet<sup>n</sup> anode & cathode of a thyristor.
- Then it is said that rate of change of voltage i.e.  $dV/dt$ .
- Such a situation is called as transient operating condition.

The current through  $C_{j2}$  is

$$I_{j2} = \frac{d(Q_{j2})}{dt} = \frac{d(C_{j2}V_{j2})}{dt}$$

$$= V_{j2} \frac{dC_{j2}}{dt} + C_{j2} \frac{dV_{j2}}{dt}$$

where

- $C_{j2}$  - capacitance of  $J_2$
- $V_{j2}$  - voltage of  $J_2$
- $Q_{j2}$  - charge in the junction.

- If the rate of rise of  $V_f$   $\frac{dV}{dt}$  is large then  $I_{j2}$  will be large. & this increases the leakage current.


- The higher leakage current causes  $(I_1 + I_2)$  tending to unity & results in SCR turn on.





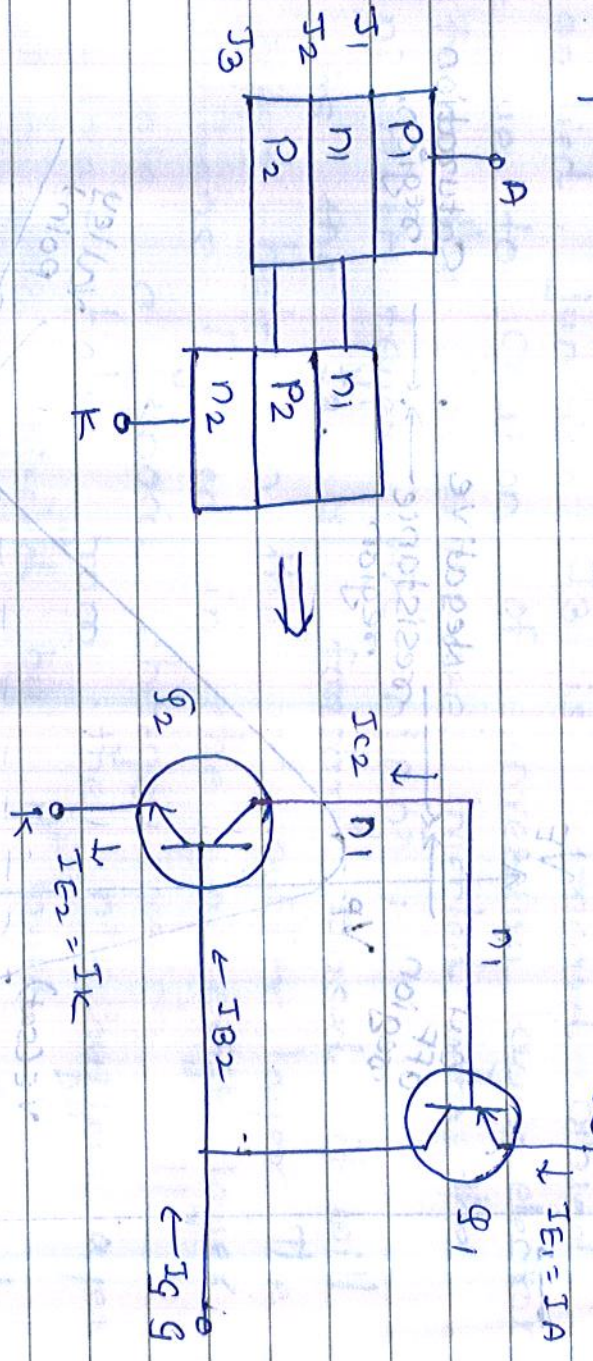
Q.3] →

Explain the two transistor analogy of SCR.




- the equivalent ckt is made up of p-n-p & n-p-n transistor.
- The anode is +ve w.r.t. cathode. & gate current is supplied.
- The gate current acts as base current for  $Q_2$  & it turns on. Its collector current  $I_{C2} = \beta_2 I_G$  starts flowing.
- But collector current of  $Q_2$  acts as base current for  $Q_1$  &  $Q_1$  starts conducting. Its collector current  $I_{C1} = \beta_1 I_{B1} = \beta_1 \beta_2 I_G$  starts to flow.
- The collector current of  $Q_1$  acts as base current of  $Q_2$  & collector current of  $Q_2$  in turn acts as base current of  $Q_1$ .
- Due to this type of connection the current multiplication takes place which is called as cumulative current multiplication & both the transistor will saturate.
- Hence SCR will get latched into on state.

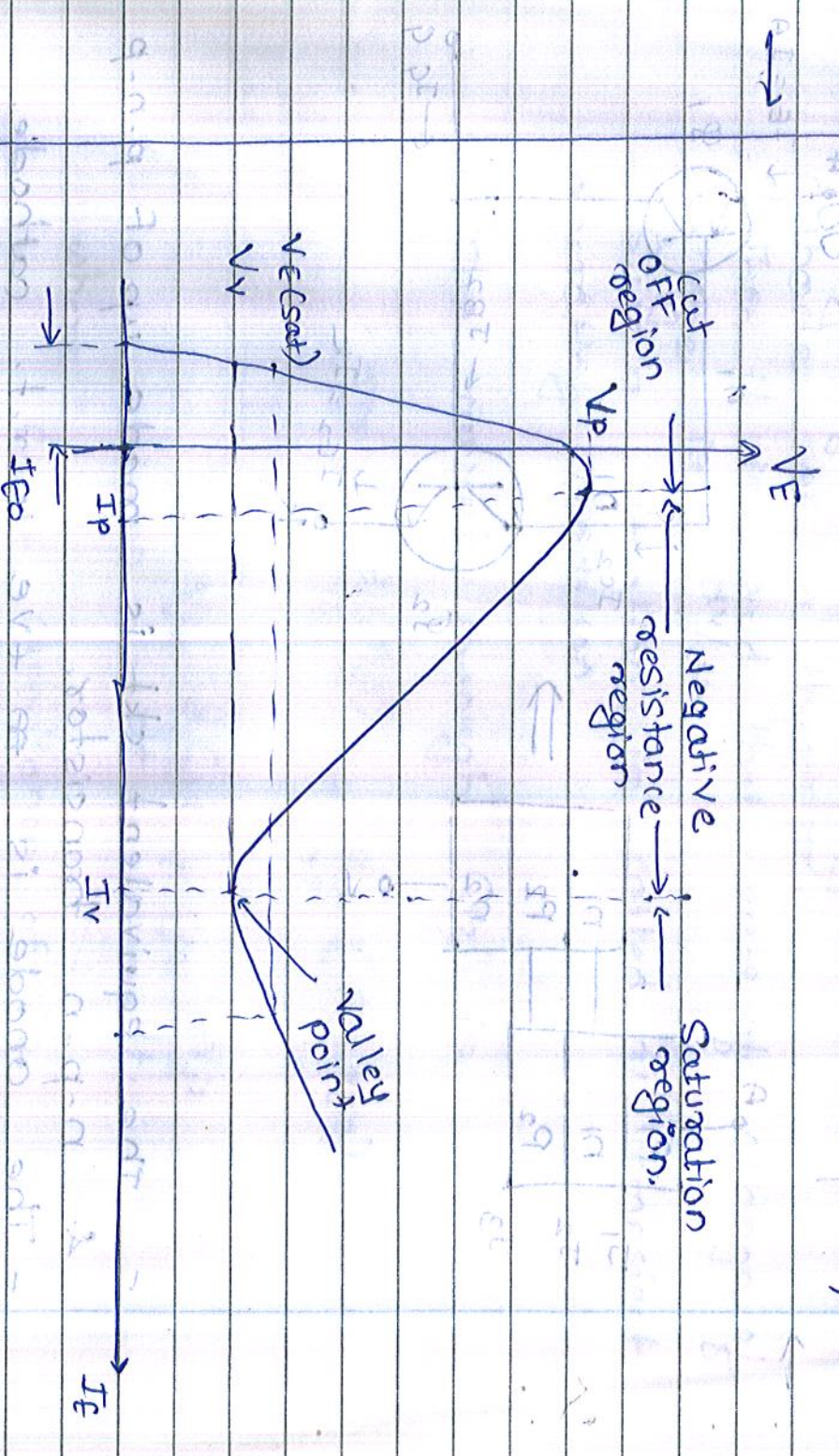Q2 b) Draw the V-I charact. of UT, & explain.




- This is a emitter vtg versus emitter current characteristics.
- when emitter vtg less than the  $V_p$ , VJT is in the OFF state & IE is not greater than  $I_{EO}$ .
- The  $I_{EO}$  corresponds to reverse leakage current. This region is known as cut off region.
- As the emitter vtg increases & reaches  $V_p$  the VJT starts conducting.
- Then with increase in emitter current  $I_E$  the emitter vtg decreases.
- This region of operation is known as negative resistance region.
- Eventually the valley point will be reached & a further increase in  $I_E$  will place the device into saturation.

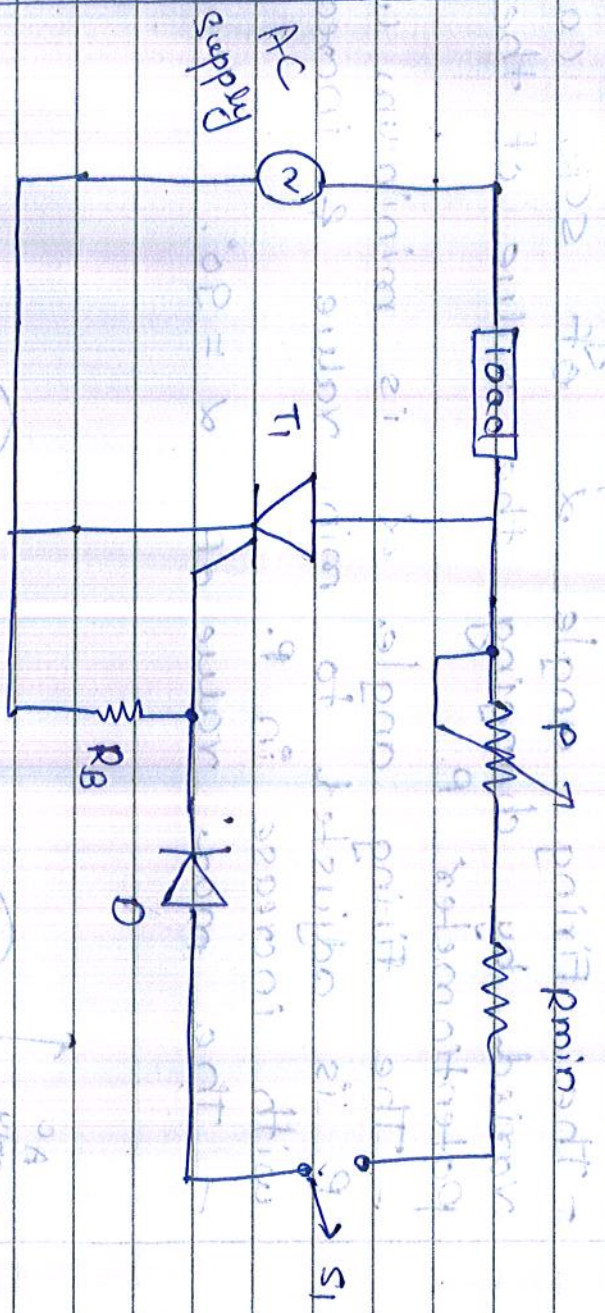3] Explain the low resistance triggering circuit for SCR.




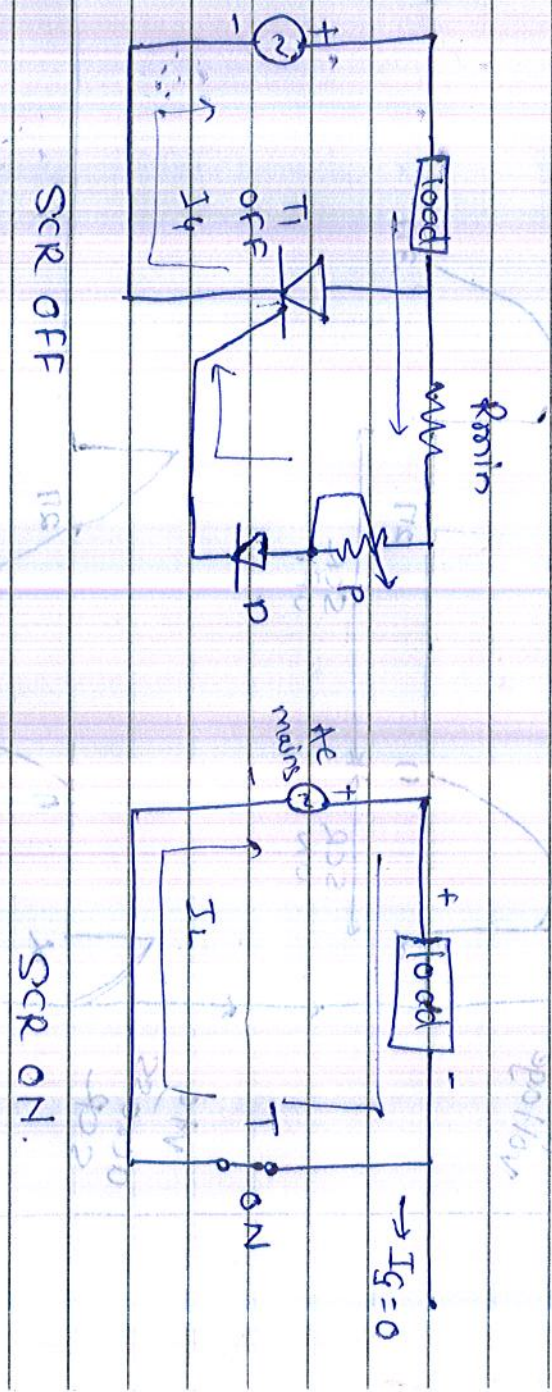- In above ckt dia. 'D' decides the value of peak gate current. The diode 'D' is used to prevent reverse voltage from being applied across the gate-cathode junction.



- In the +ve half cycle of AC supply, the current flows through P, D, Rmin & gate-cathode junction of SCR.
- When SCR is turned ON, the voltage across it reduces to its conduction drop value, which is a very small value. The gate current is then almost zero.

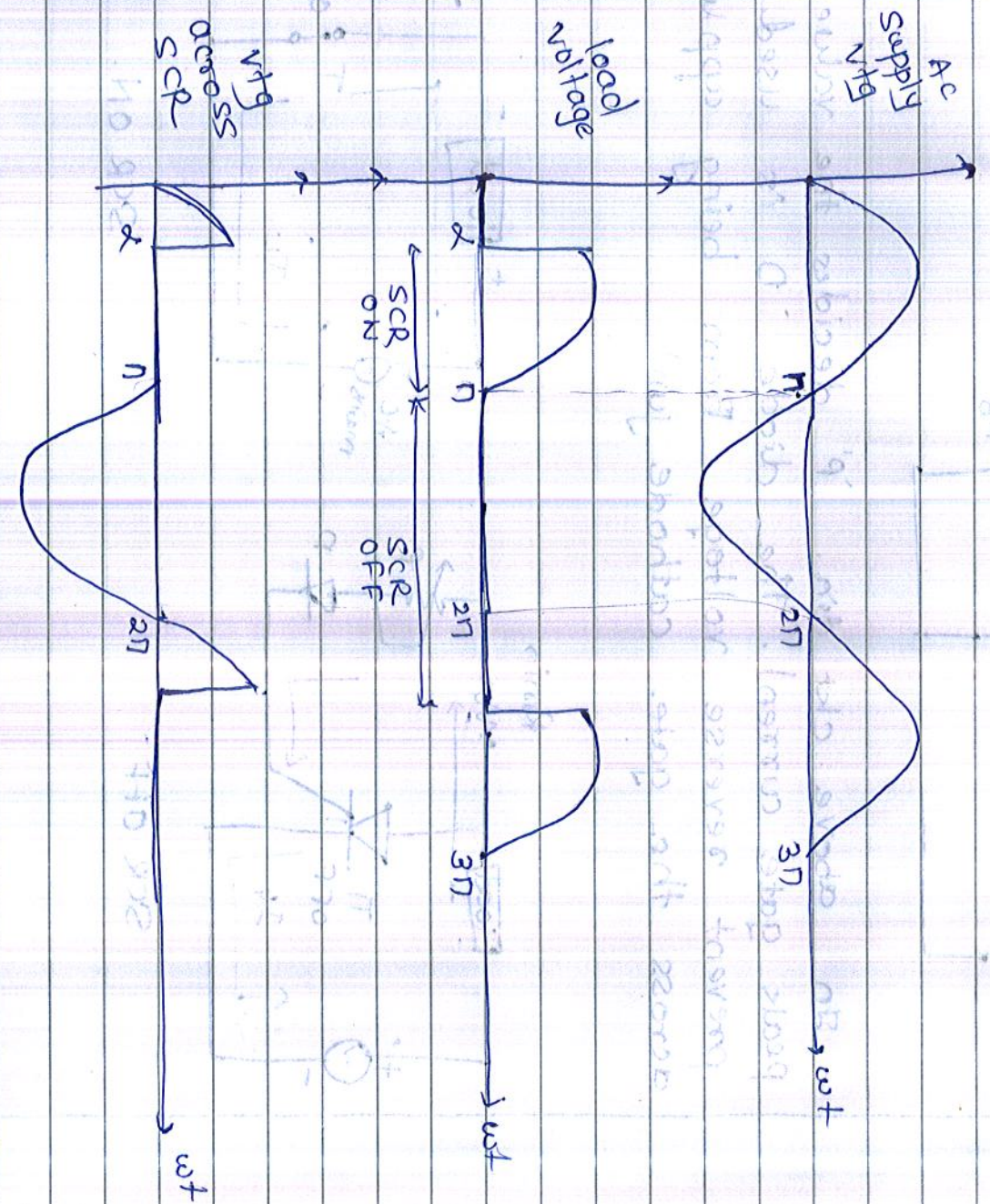- The SCR continues to conduct upto  $\pi$  radians. if load is purely resistive.
- The firing angle  $\alpha$  of SCR can be varied by changing the value of the potentiometer  $P$ .
- The firing angle  $\alpha$  is minimum when  $P$  is adjusted to min. value & increases with increase in  $P$ .
- The max. value of  $\alpha = 90^\circ$ .



add voltage ON to stop turn SVT out OE -  
 stop & turn Q & g. adjust 200g. 700000  
 22000 pfr anti. no. 802 to 901 shorten  
 to other jobs. 21 at 100000 41  
 with pi. 100000 stop. 211. 100000 100000  
 100000 100000